



February, 1988

Philip Karantzalis

To illustrate the performance difference between a low-pass passive R, C loop filter and the LTC1062, the circuit of Figure 2 was tested for a PLL with a $60\text{Hz} \pm 10\%$ input fre-

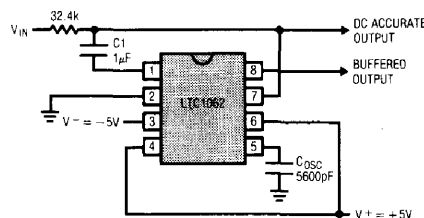


Figure 1.8Hz 5th Order Butterworth Lowpass Filter


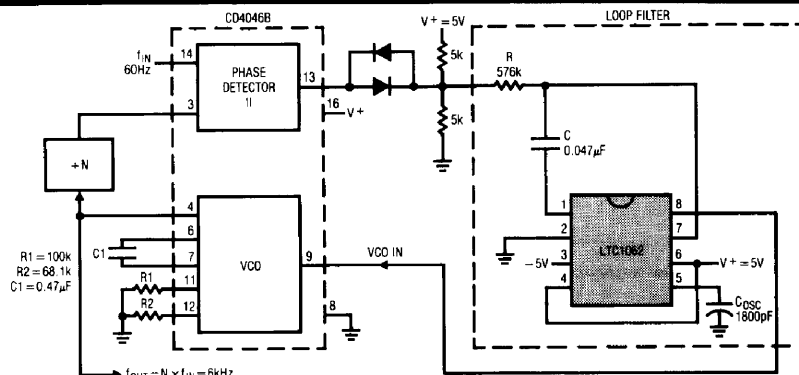


Figure 2

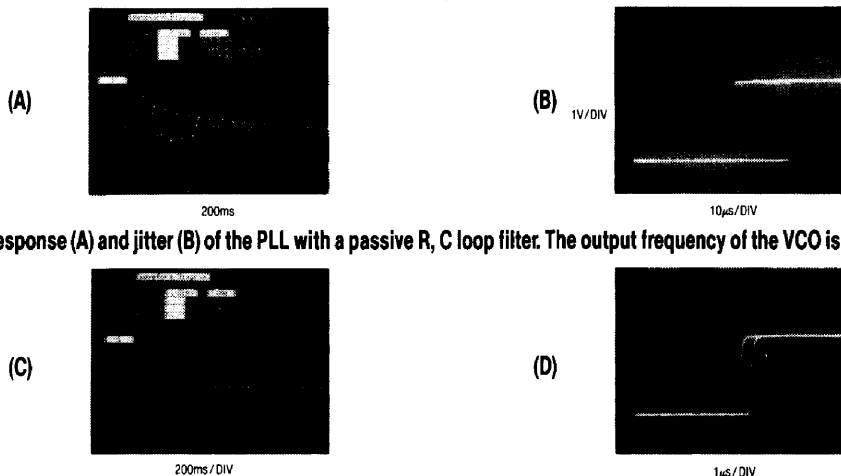

Transient response (A) and jitter (B) of the PLL with a passive R, C loop filter. The output frequency of the VCO is 6kHz and the $+N = 100$.

Transient response (C) and jitter (D) of the PLL with the LTC1062 used as a loop filter. The VCO output frequency is 6kHz and the $+N = 100$. The jitter is reduced to the internal jitter of the VCO.

Figure 3

quency range and with $+N = 100$. Then, the PLL's VCO output could be used to drive the clock input of a precision switched capacitor filter, such as an LTC1060A set up in a 100:1 clock to center ratio, and configured as a 60Hz sharp notch or bandpass filter. Figure 3A shows the transient response of the loop when a passive R,C loop filter, Figure 4, is used. The input frequency is shifted from 54Hz to 60Hz and the loop takes 820ms to settle within 5% of its steady state value. The corner frequency of the R, C passive filter is 22Hz. The natural frequency of the loop is approximately 10Hz and the damping factor less than 0.1. Figure 3B shows the jitter at the VCO output under the above conditions. A $30\mu\text{s}$ jitter with $f_{OUT} = 6\text{kHz}$ corresponds to 18% instantaneous frequency inaccuracy. This makes the PLL VCO output unusable as a

clock generator for a tracking switched capacitor filter. A small improvement in the VCO output jitter could be achieved by further decreasing the filter's cutoff frequency; this, however, would further penalize the circuit's settling time.

Figures 3C and 3D show the PLL performance when an LTC1062 is used as a loop filter. The corner frequency f_c of the LTC1062 was set at 9.5Hz ($\approx 1/6 f_{IN}$) and its internal clock was set for 2.4kHz ($\approx 252 \times f_c$). The settling time of the loop was 320ms and the damping factor was optimally set to 0.7. The $1\mu\text{s}$ VCO output jitter, $f_{OUT} = 6\text{kHz}$, was measured over 5 periods and it is attributed to the inherited jitter of the VCO internal circuitry. With the LTC1062 used as a loop filter, the circuit's jitter corresponds to 0.12% frequency error. This is quite adequate to drive the clock input of 0.3% accurate switched capacitor filters, such as LTC1059A or LTC1060A.

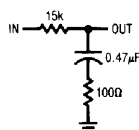


Figure 4. Lowpass R, C Filters used for PLL Example

For Filter literature call 800-637-5545. For help with an application call (408) 432-1900, Ext. 361.